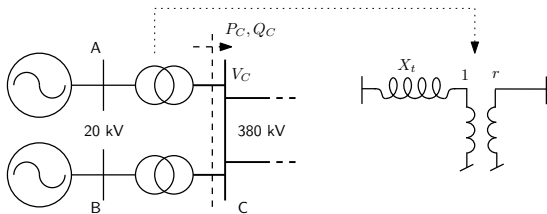


A power plant connected to a 380-kV network is made up of two identical generators with the following characteristics :

- nominal apparent power of synchronous machine : 250 MVA
- nominal voltage : 20 kV
- nominal power of turbine : 230 MW
- stator resistance :  $R_a = 0.005$  pu
- synchronous reactance :  $X_m = 2.15$  pu
- when the generator operates at no load (i.e. with stator opened), under its nominal voltage, the field voltage  $v_f$  is 500 V and the field current  $i_f$  is 670 A
- under the nominal voltage, the capability curves relative to respectively the nominal turbine power, the maximum rotor current and the maximum stator current cross each other at a single point.



Each transformer can be modeled as shown in the figure, with the following parameters :

- nominal apparent power : 250 MVA
- open-circuit voltages : 20 / 397.1 kV
- leakage reactance :  $X_t = 0.15$  pu on the (20 kV, 250 MVA) base.

Consider the following operating point :

- voltage at bus C : 395.2 kV
- powers injected received at bus C :  $P_C = 380$  MW,  $Q_C = 70$  Mvar
- both machines produce the same powers.

Determine :

- 1 the voltage at bus A (in kV)
- 2 the reactive power produced by each machine (in Mvar)
- 3 the field voltage (in V) and field current (in A) of each machine
- 4 the power balance of each machine
- 5 the reactive power reserve of each machine (in Mvar). Neglect  $R_a$

using the following base voltages and power : 20 kV, 380 kV, 100 MVA